
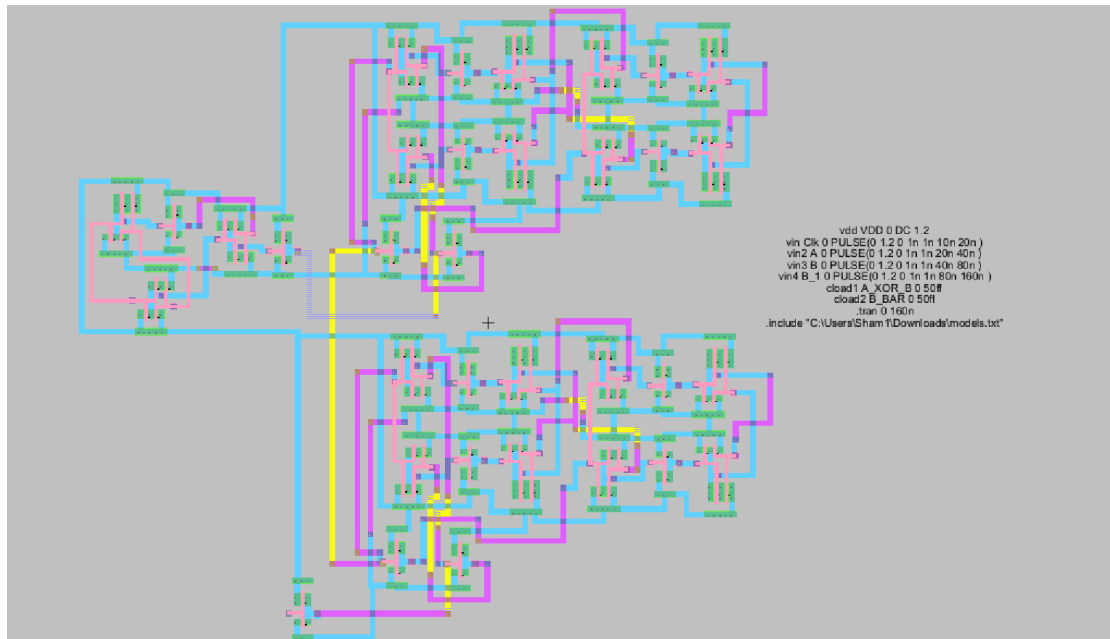


Layout Level:


1)Counter:

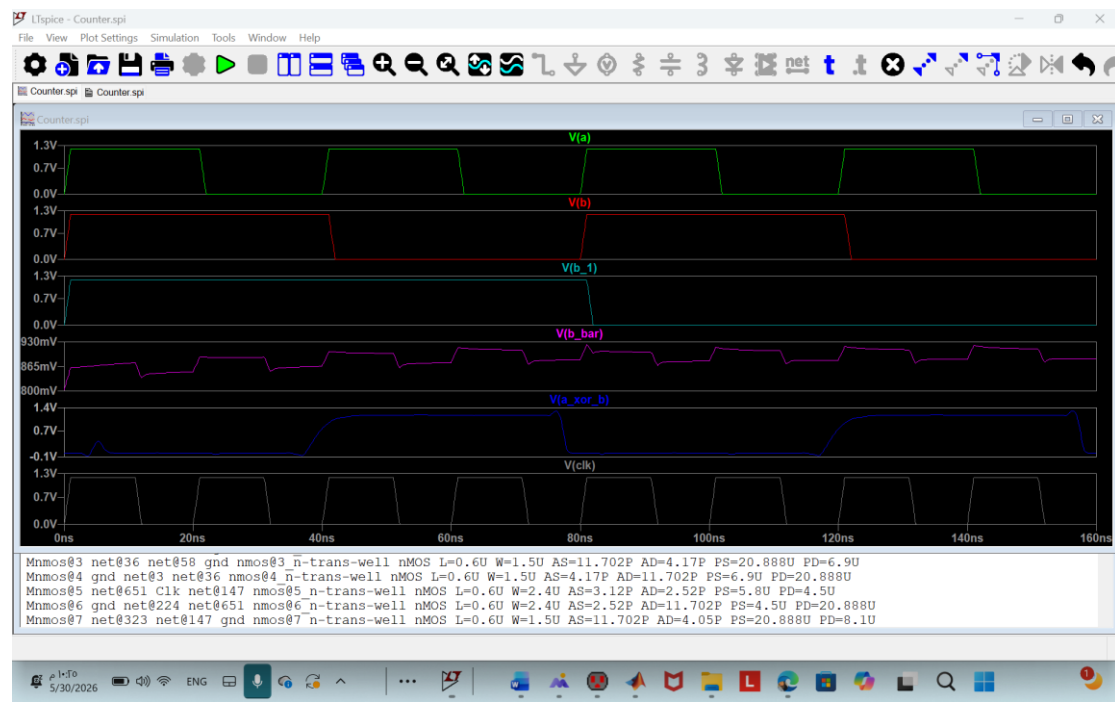


Waveform:




2)Decoder:

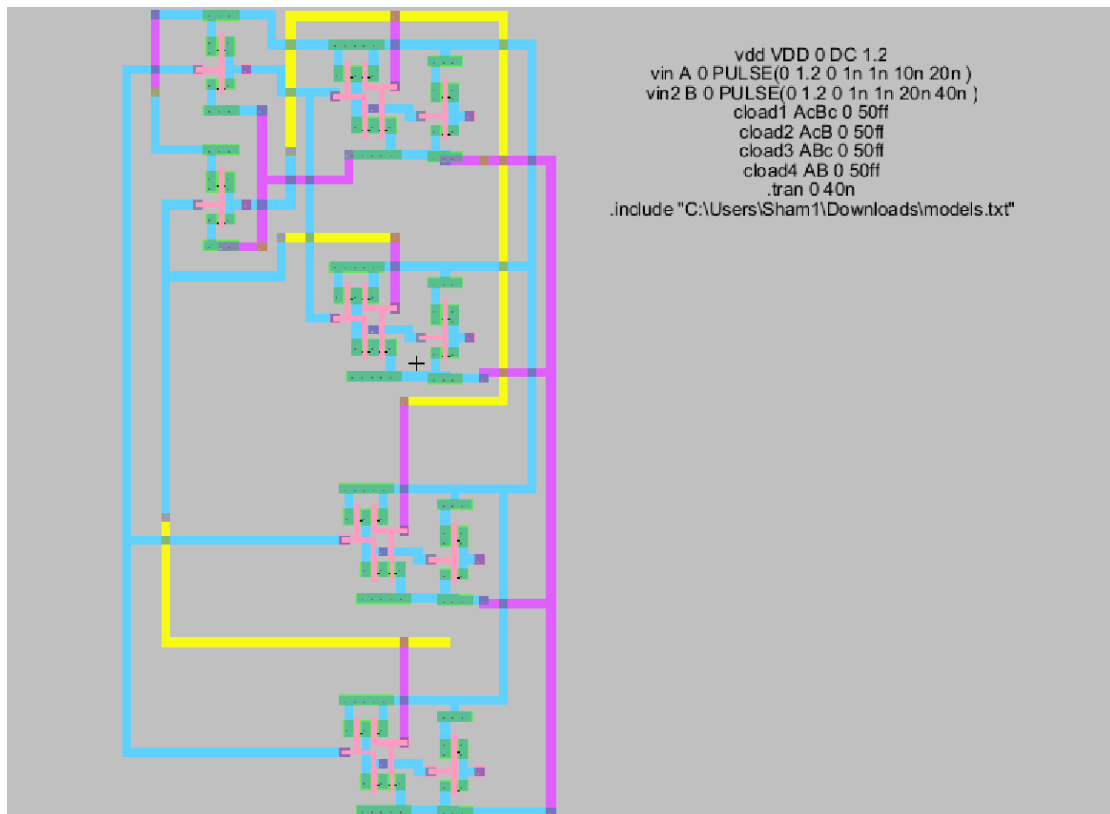


Waveform:

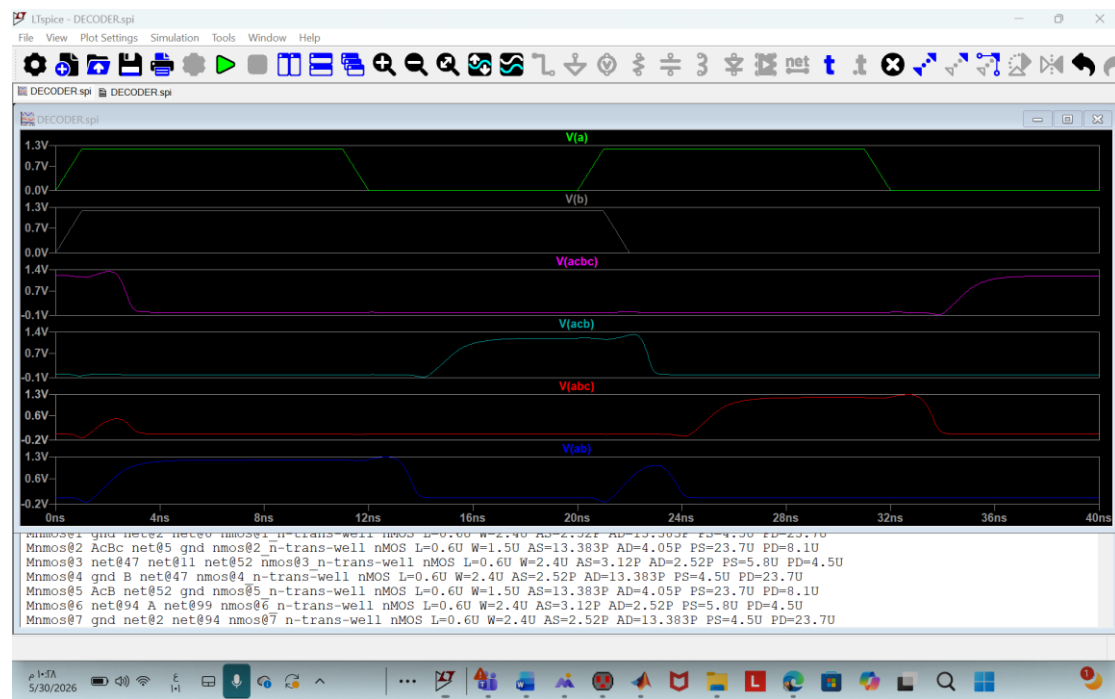


3)SRAM:

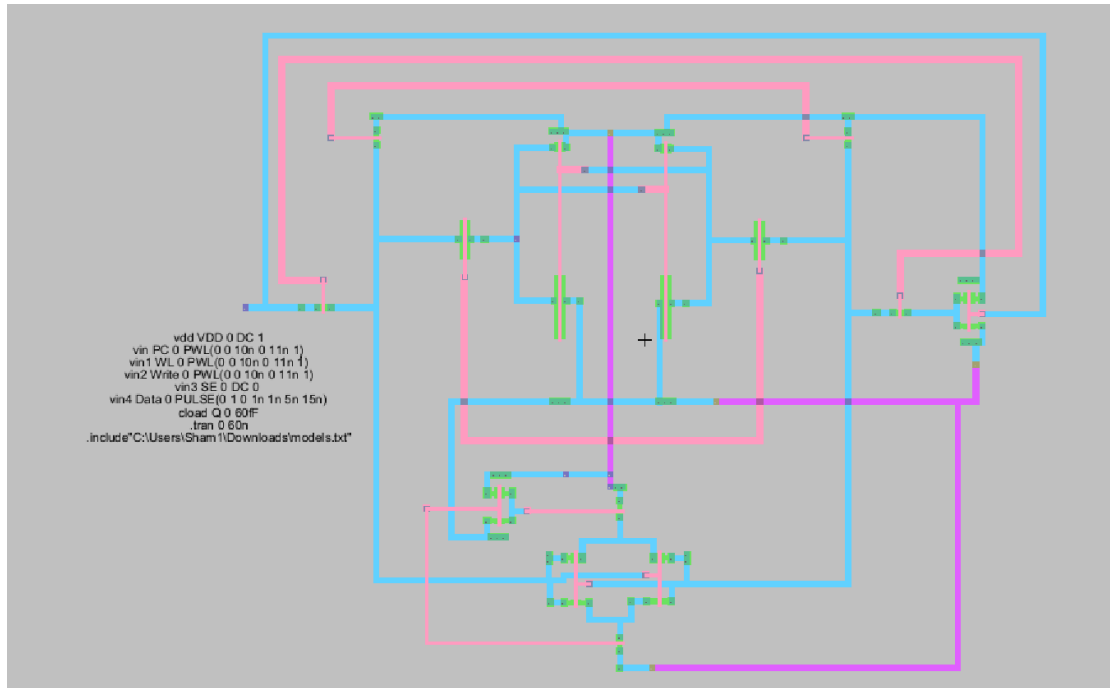


Waveform:

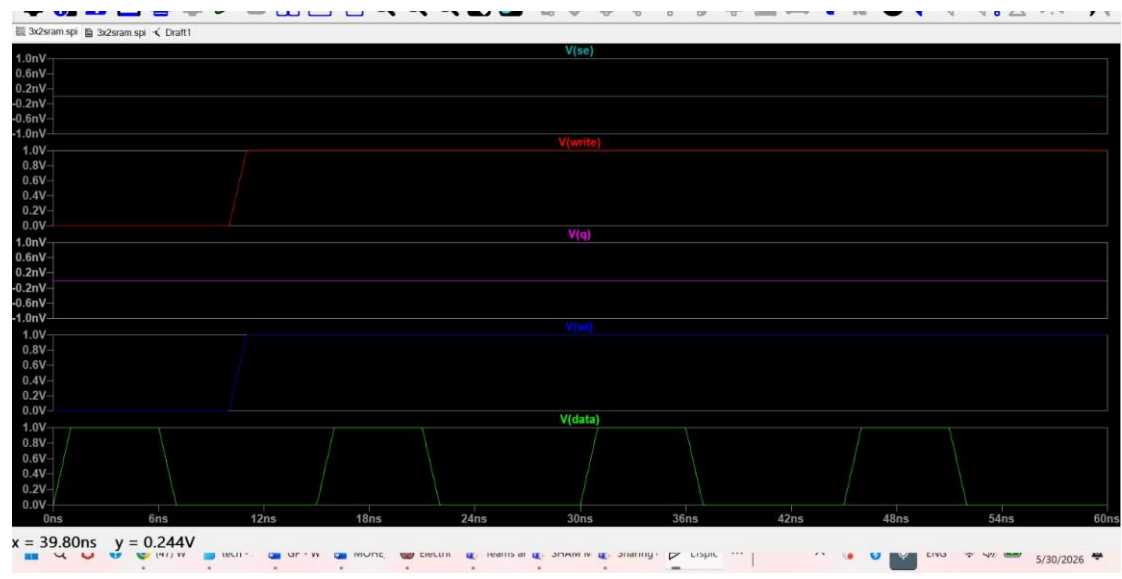


4)SRAM 2×3 :

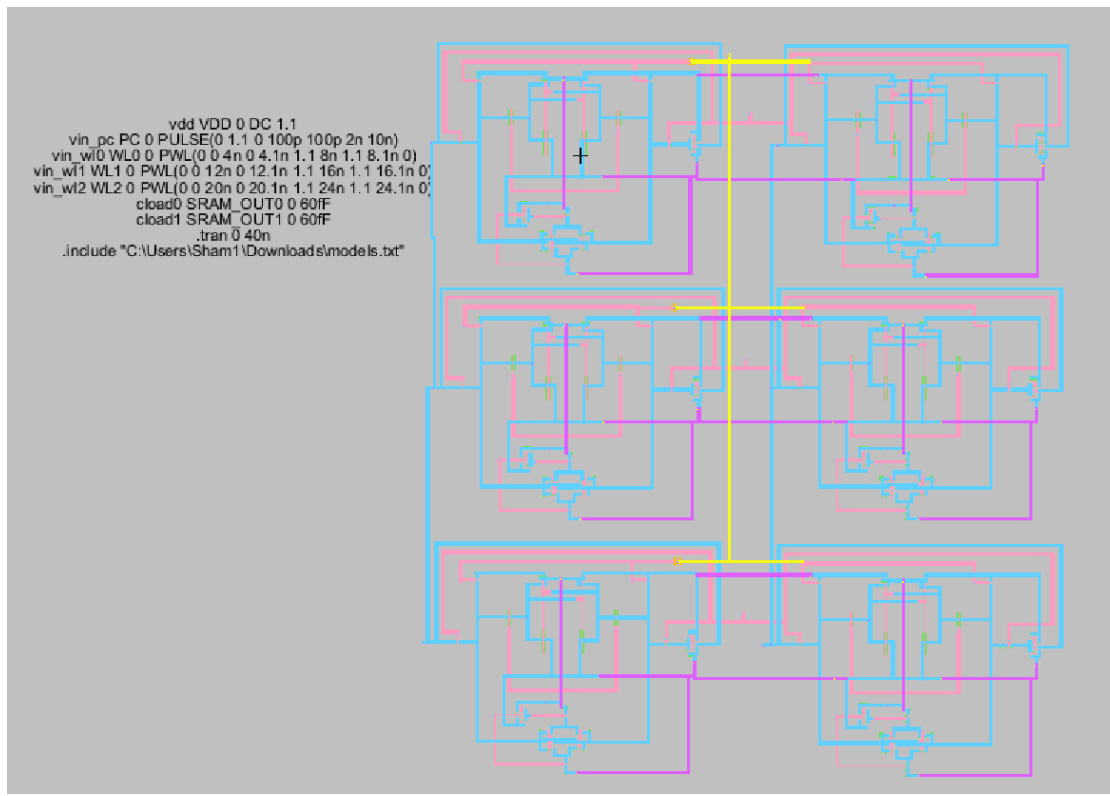


5)D_FF

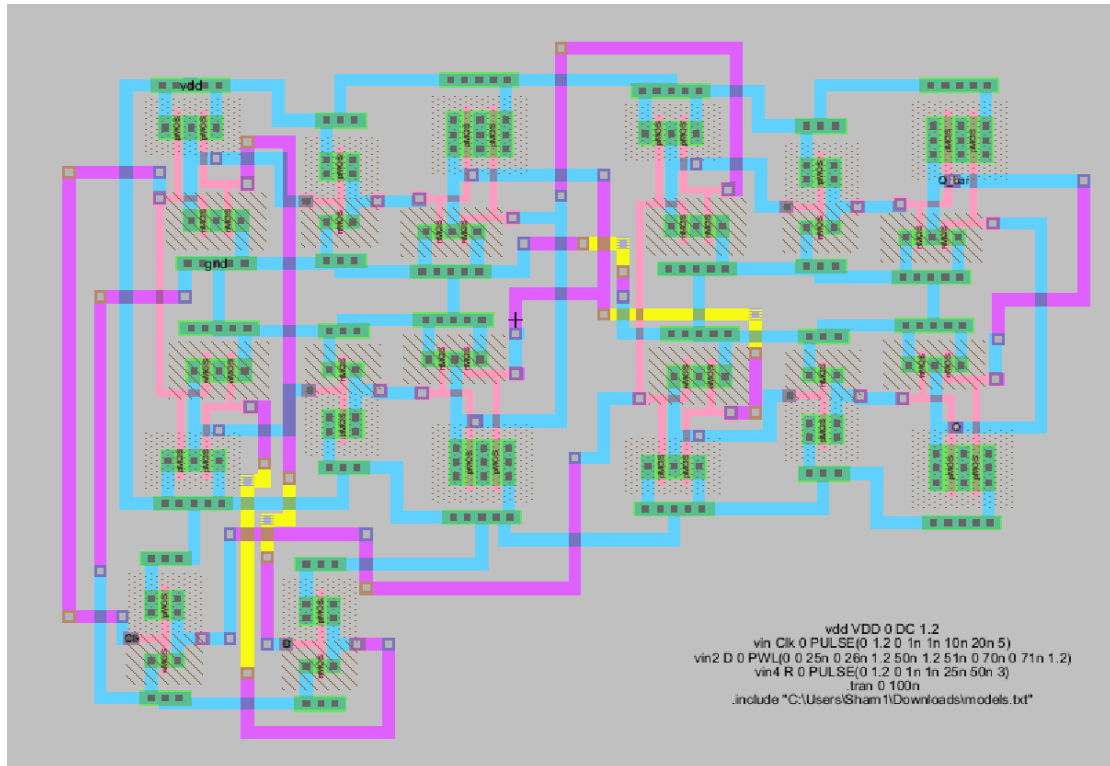


Waveform:

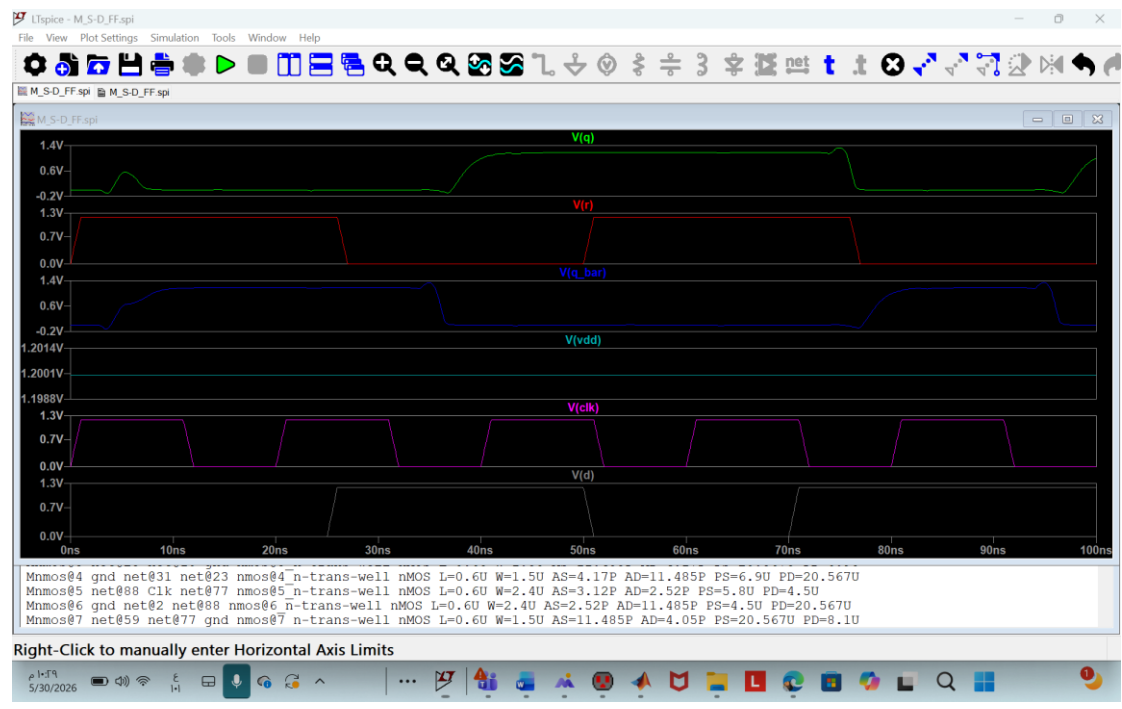

6)HA:

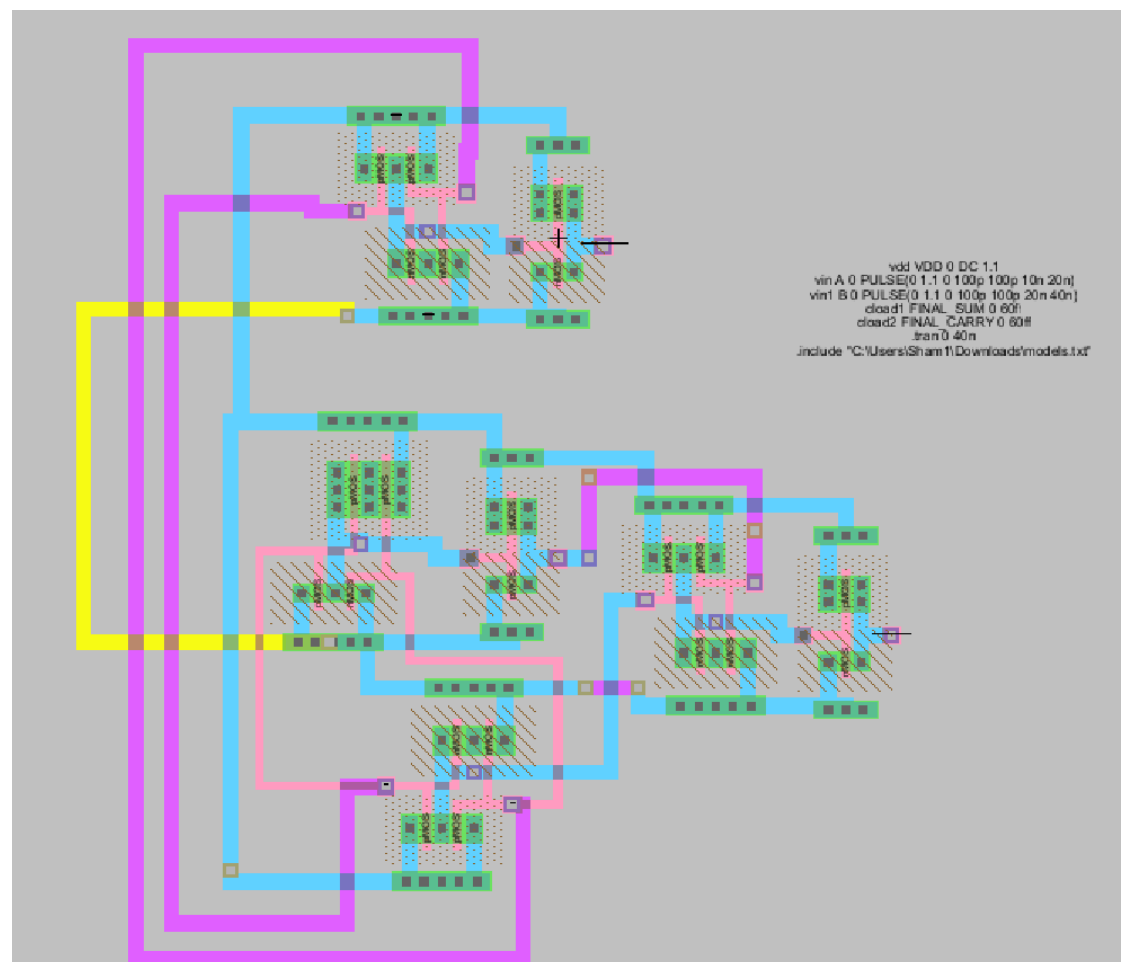

Waveform:

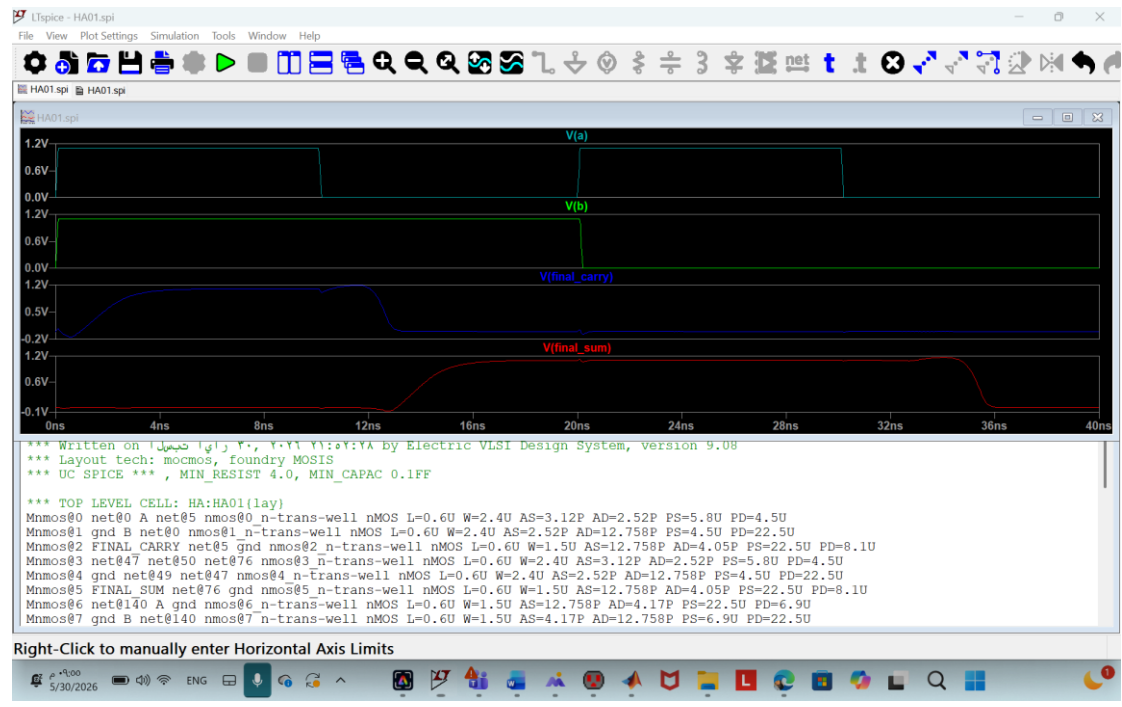

7)Top_Level :

